
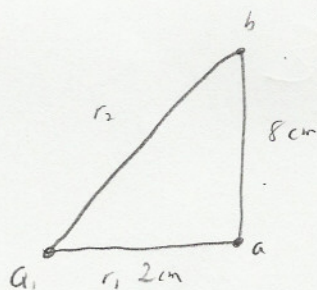


Problem 1. Figure 1 shows the location of two positively charged particles, Q_1 and Q_2 . The particle denoted Q_1 has a positive charge of 10 nC and the particle denoted Q_2 has a positive charge of 5 nC. The two particles have (x,y) coordinates (2,2) and (10,10) respectively, where each coordinate has units centimeters.

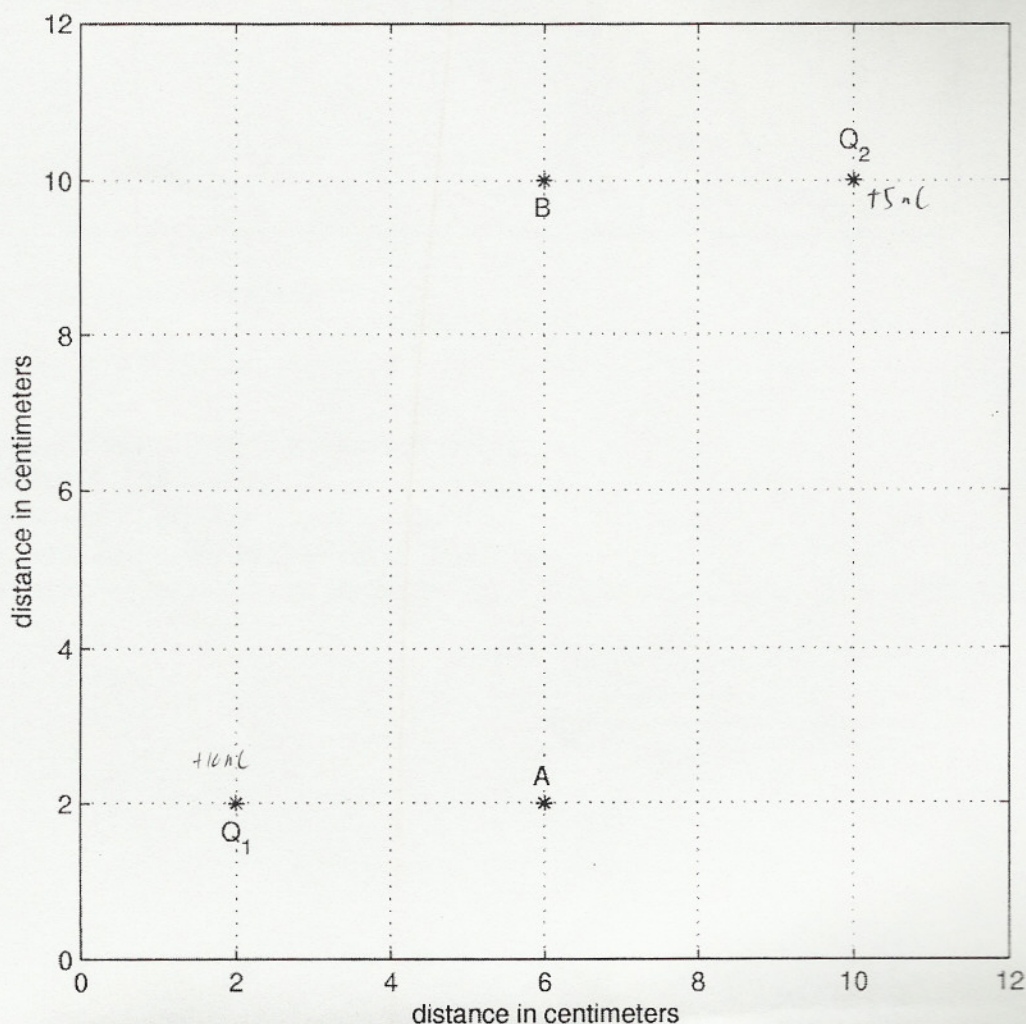- a) How much work is required to move a test charge of 2 mC from point A to point B [point A has coordinates (6,2) and point B has coordinates (6,10)]? (3 marks)
 b) What is V_{BA} ? (3 marks)



$$r_2 = \sqrt{2^2 + 8^2}$$

$$r_2 = 8.24 \text{ cm}$$

$$r_2 = 0.0824 \text{ m}$$

$$A) \quad W_1 = k \cdot Q_1 \cdot Q_t \left/ \frac{r_2 - r_1}{r_2 \cdot r_1} \right|$$

$$W_1 = (9.0 \times 10^9) (10 \times 10^{-6}) (2 \times 10^{-3}) \left/ \frac{0.0824 - 0.02}{0.165} \right|$$

$$W_1 = 68.1 \text{ J}$$

N_{11} time left

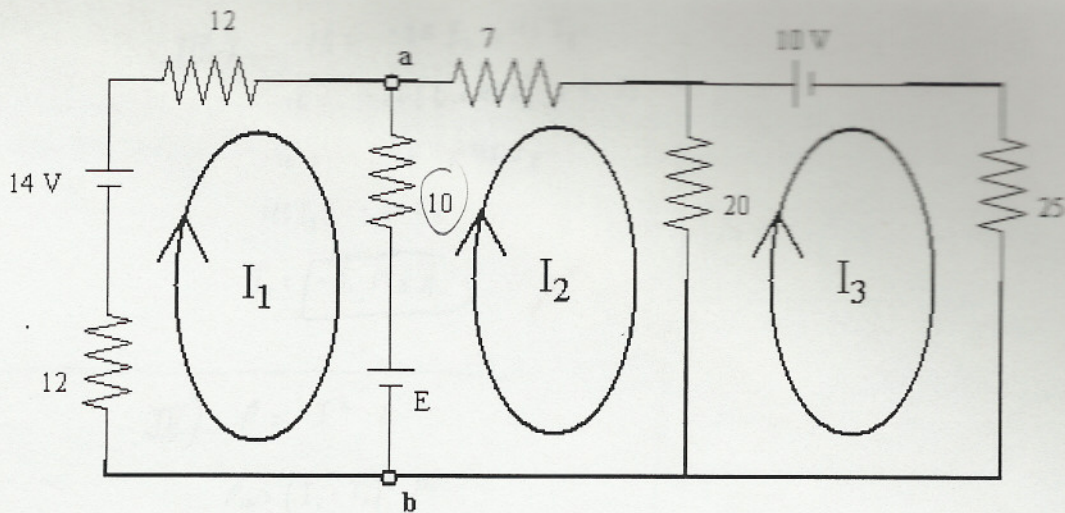


Figure 2 (all resistances are in Ohms)

Given $I_1 = 0.323 \text{ A}$ and $I_2 = 0.099 \text{ A}$:

- What is the voltage across the 10Ω resistor? (3 marks)
- What is the voltage V_{ab} ? (3 marks)
- What is the current I_3 ? (3 marks)
- What is power dissipated in the 10Ω resistor? (3 marks)
- Write the loop equations for the circuit shown in Figure 2. Use the matrix template given below. (3 marks)

$V_{10\Omega} = 2.24 \text{ V}$	$I_3 = -0.178 \text{ A}$
$V_{ab} = 9.48 \text{ V}$	Power $_{10\Omega} = 0.502 \text{ W}$
Equations	

$$\begin{pmatrix} 24 & -10 & 0 \\ -10 & 17 & -20 \\ 0 & -20 & 45 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 6.762 \\ 7.238 \\ -10 \end{pmatrix}$$

$$14 - E = I_1(12 + 12) - I_2(10)$$

$$\textcircled{1} 14 - E = 24I_1 - 10I_2$$

$$E = I_2(10 + 7) - I_1(10) - I_3(20)$$

$$E = 17I_2 - 10I_1 - 20I_3$$

$$\textcircled{2} E = -10I_1 + 17I_2 - 20I_3$$

$$-10 \text{ V} = I_2(20 + 25) - I_3(20)$$

$$-10 = 45I_3 - 20I_2$$

$$-10 = -20I_2 + 45I_3$$

$$14 - E = 24I_1 - 10I_2$$

$$14 - E = 24(0.323) - 10(0.099)$$

$$14 - E = 7.752 - 0.99$$

$$-E = -7.238$$

$$E = 7.238 \text{ V}$$

$$I) V_{10\Omega} = I_1 R$$

$$V_{10\Omega} = (I_1 - I_2) R$$

$$V_{10\Omega} = (0.323 - 0.099)(10)$$

$$V_{10\Omega} = 2.24 \text{ V}$$

$$II) V_{ab} = V_E + V_O$$

$$V_{ab} = E + I R_O$$

$$V_{ab} = (7.238 \text{ V}) + (I_1 - I_2) R_{10}$$

$$V_{ab} = (7.238 \text{ V}) + 2.24 \text{ V}$$

$$V_{ab} = 9.478 \text{ V}$$

$$V_{ab} = 9.48 \text{ V}$$

- a) Write the nodal equations for the circuit shown in Figure 3. Use the matrix template given below. (3 marks)
- b) Solve for the voltages V_1 and V_2 . (3 marks)
- c) Find the magnitude and direction of the current through the $3\text{-}\Omega$ resistor. (3 marks)
- d) Find the magnitude and direction of the current through the $6\text{-}\Omega$ resistor. (3 marks)

$V_1 =$ 0.728 V	$I_{3\Omega} =$ 0.477 A	Direction of $I_{3\Omega}$ Circle the correct answer Left <input type="radio"/> Right <input checked="" type="radio"/>
$V_2 =$ 1.28 V	$I_{6\Omega} =$ 0.6920 A	Direction of $I_{6\Omega}$ Circle the correct answer Left <input type="radio"/> Right <input checked="" type="radio"/>


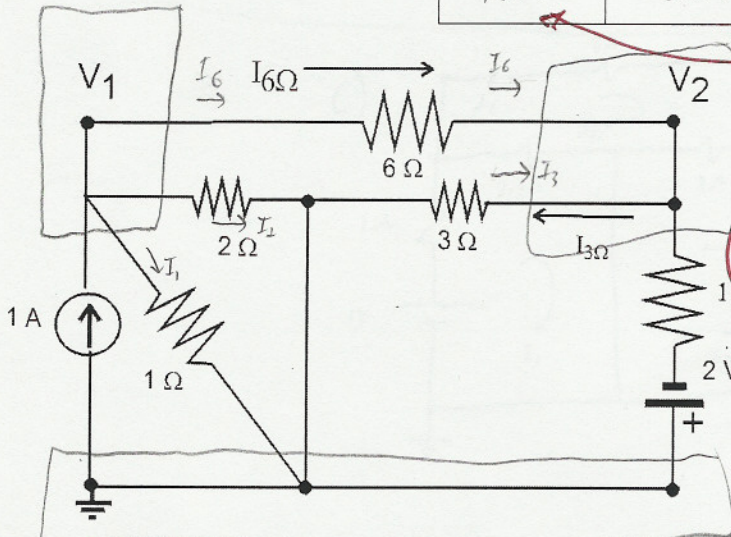


Figure 3.

ref

Conflict here!

3

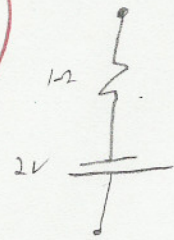

$$I = \frac{V}{R} = \frac{2\text{ V}}{1\Omega} = 2\text{ A}$$

$$\begin{pmatrix} \frac{5}{3} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{3}{2} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 1 \\ 2 \end{pmatrix}$$

A) $I_{in} = I_{out}$
 $1\text{ A} = I_1 + I_2 + I_6$
 $1 = \frac{V_1}{1} + \frac{V_1}{2} + \frac{V_{12}}{6}$

$$1 = V_1 + \frac{1}{2}V_1 + \frac{1}{6}V_1 - \frac{1}{6}V_2$$

$$1 = V_1(1 + \frac{1}{2} + \frac{1}{6}) - \frac{1}{6}V_2$$

$$1 = \frac{10}{6}V_1 - \frac{1}{6}V_2$$

$$1 = \frac{5}{3}V_1 - \frac{1}{6}V_2$$

$$I_{out} = I_{in}$$

$$2\text{ A} = I_4 + I_3 + I_6$$

$$2 = \frac{V_2}{1} + \frac{V_2}{3} + \frac{V_{21}}{6}$$

$$2 = V_2 + \frac{1}{3}V_2 + \frac{1}{6}V_2 - \frac{1}{6}V_1$$

$$2 = V_2(1 + \frac{1}{3} + \frac{1}{6}) - \frac{1}{6}V_1$$

$$2 = \frac{3}{2}V_2 - \frac{1}{6}V_1$$

Algebra and error

B) $1 = \frac{5}{3}V_1 - \frac{1}{6}V_2$

$$2 = \frac{3}{2}V_2 - \frac{1}{6}(\frac{3}{5} + \frac{1}{6}V_2)$$

$$\frac{3}{2}V_2 = \frac{3}{5} - \frac{1}{6}V_2$$

$$V_1 = \frac{3}{5} + \frac{1}{6}(1.28)$$

$$V_1 = 0.728\text{ V}$$

Problem 4. Using superposition (Figure 4), find

- the current through the $2\text{-}\Omega$ resistor due to the voltage source. (3 marks)
- the current through the $2\text{-}\Omega$ resistor due to the current source. (3 marks)
- the power dissipated by the $2\text{-}\Omega$ resistor. (3 marks)

$I_{2\Omega}(\text{volt. source}) = 0.3 \text{ A}$	$I_{2\Omega}(\text{curr. source}) = 0.958 \text{ A}$	$P_{2\Omega} = 3.17 \text{ W}$
--	--	--------------------------------


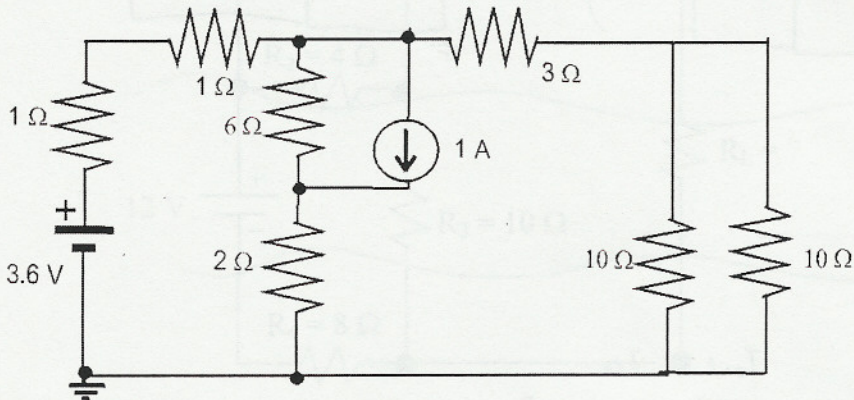


Figure 4.

Voltage Source

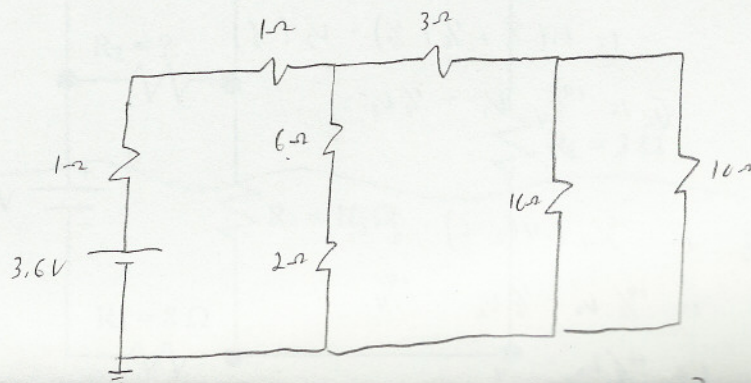


$$R_A = (1\Omega) + (1\Omega)$$

$$R_A = 2\Omega$$

$$R_B = (3\Omega) + [(10\Omega) \parallel (10\Omega)]$$

$$R_B = (3\Omega) + (5\Omega)$$

$$R_B = 8\Omega$$

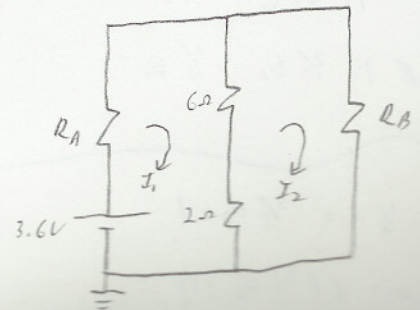

$$3.6\text{V} = I_1(2 + 8) - I_2(2 + 6)$$

$$\textcircled{1} 3.6 = 10I_1 - 8I_2$$

$$0 = I_2(8 + 6) - I_1(6 + 2)$$

$$\textcircled{2} 0 = 16I_2 - 8I_1$$

$$\textcircled{1} 10I_1 = 3.6 + 8I_2$$

$$I_1 = 0.36 + 0.8I_2$$

$$\textcircled{2} 0 = 16I_2 - 8(0.36 + 0.8I_2)$$

$$0 = 16I_2 - 2.88 - 6.4I_2$$

$$2.88 = 9.6I_2$$

$$I_2 = 0.3 \text{ A}$$

$$\textcircled{1} I_1 = 0.36 + 0.8I_2$$

$$I_1 = 0.36 + 0.8(0.3)$$

$$I_1 = 0.36 + 0.24$$

$$I_1 = 0.6 \text{ A}$$


$$I_{2\Omega} = I_1 - I_2$$

3


Problem 5. In the circuits shown below, the objective is to achieve maximum power dissipation by the load resistor R_L in each case.

Part a	Part b
$R_L = 5 \Omega$	$R_2 = 2.75 \Omega$



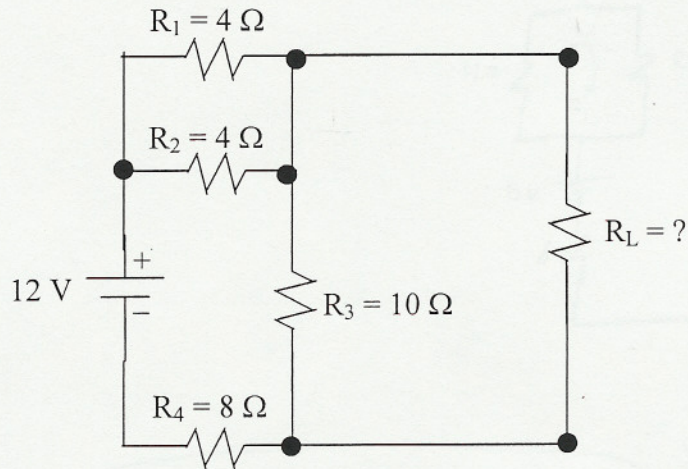
- (a) What is the value of R_L for maximum power dissipation by R_L ? (3 marks)



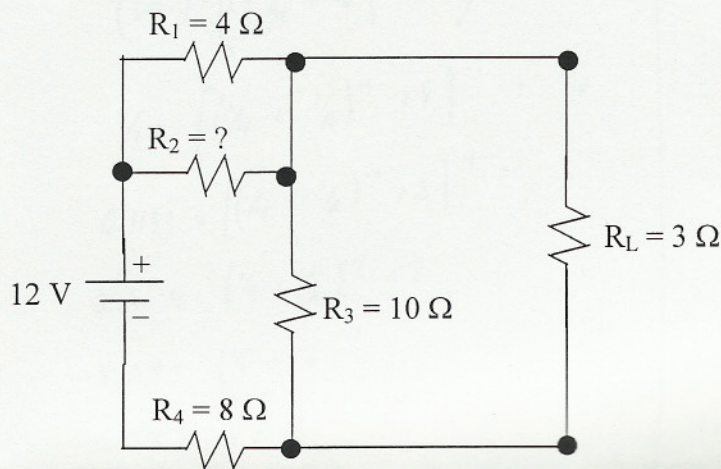- (b) What is the value of R_2 if there is maximum power dissipation by R_L (3Ω)? (3 marks)



A) $R_L = R_{Th}$ for max power

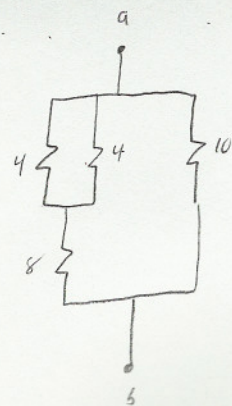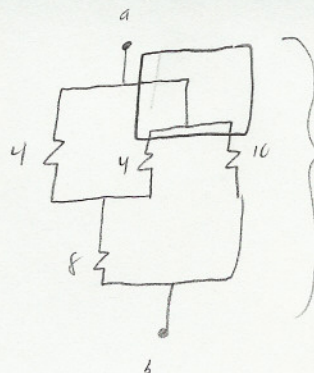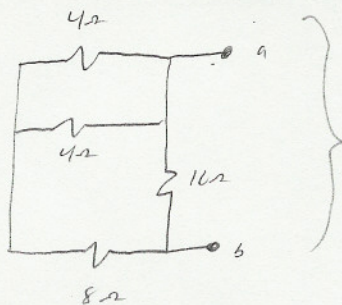


$$R_{Th} = \left[\left(\frac{4\Omega}{1} \parallel \frac{4\Omega}{1} \right) + 8\Omega \right] \parallel 10\Omega$$

$$R_{Th} = \left[\frac{2\Omega}{1} + 8\Omega \right] \parallel 10\Omega$$


Problem 6.

- Determine the Thévenin equivalent circuit between terminals "a" and "b" for the circuit shown below.
i.e. what is R_{Th} and E_{Th} ? (6 marks)
- Draw the Thévenin equivalent circuit, you are to clearly indicate the polarity of the battery and the terminals "a" and "b". (3 marks)

$R_{Th} = 9\Omega$	$E_{Th} = 8V$
Thévenin circuit	

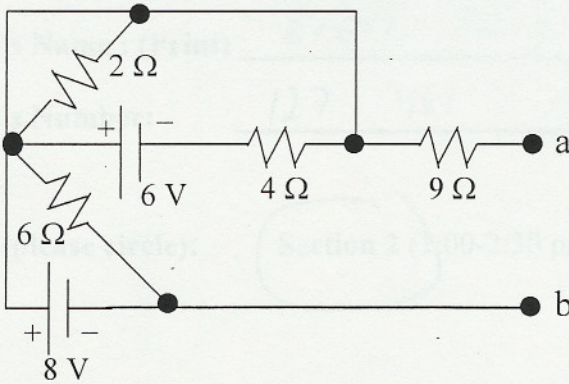


R_{Th}

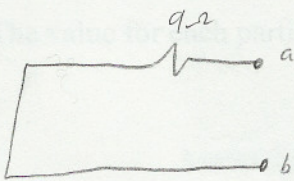

$R_{Th} = 9\Omega$

$E_{Th} = 8V$

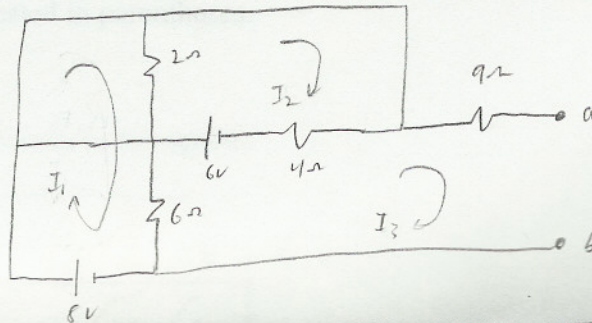

$8V = I_1(2+6) - I_2(2)$

① $8 = 8I_1 - 2I_2$

② $I_3 = 0$

$6V = I_2(2+6) - I_1(2)$

③ $6 = 8I_2 - 2I_1$

① $8 = 8I_1 - 2I_2$

$8I_1 = 8 - 2I_2$

$I_1 = 1 - \frac{1}{4}I_2$

③ $6 = 8I_2 - 2(1 - \frac{1}{4}I_2)$

$6 = 8I_2 - 2 + \frac{1}{2}I_2$

$8 = \frac{15}{2}I_2$

$I_2 = \frac{16}{15}$

$E_{Th} = V_{ab} = 8V$

$R_{Th} = 9\Omega$

